Roberts RIC. 1

1884

Solid state portable radio receiver

Introduction

An outstanding feature of the Roberts RIC. 1 battery operated radio receiver is the incorporation of an integrated circuit device, a small capsule containing a micro-circuit of eleven transistors, eleven resistors and a diode. The familiar i.f. amplifier has disappeared, and the required degree of selectivity is achieved by means of a

Wavebands covered are m.w. 182-555m (1,648-540kc/s) and l.w. 1,160-2,000m (259-150kc/s), reception is via either the internal ferrite rod aerial assembly or a car-type aerial for which a single point co-axial socket is fitted at the top of the case adjacent to the volume control knob.

Complementary symmetry is employed in the three transistor a.f. amplifier which drives a 7in by 3½in 5Ω elliptical loudspeaker which provides an audio output power in excess of 1W. A normally closed miniature jack located at the top of the case adjacent to the tuning control knob enables an earphone to be connected for personal listening, at the same time muting the internal

Operating power is supplied by a 9V battery Ever Ready type PP9 or its equivalent.

Voltage analysis

Voltages quoted in the table, col. 3, were obtained from data supplied by the manufacturers and are all positive with respect to battery negative. There was no signal input, the volume control was at minimum and they were measured on a 20,000 Ω/V meter.

(Continued overleaf - col. 1)

Resiste	ors	
Resiste R1 R2 R3 R4 R5 R6 R7 R8 R9 R10 R11	8-2kΩ 150Ω 820Ω 8-2kΩ 390Ω 4-7kΩ 3-3kΩ 27kΩ 390Ω 10kΩ 180Ω	B2 B1 B2 B2 B2 B2 B2 B2 B2 B2 B2
R12 R13 R14 R15 R16 R17 R18 RV1 RV2 RV3	470Ω 12Ω 82kΩ 470Ω 8·2kΩ 390Ω 15kΩ 22kΩ 220Ω 22kΩ	B2 B2 B2 B2 B2 B2 B2 B2 B2 B2 B2


Capa	citors		C15	400µF	B2
			C16	0.047µF	B2
C1	10µF	B2	C17	32µF	B2
C2	0-1 µF	B1	C18	0.01 µF	B2
C3	0.047 uF	B2	C19	640µF	B2
C4	0.047µF	B2	CV1	207pF	B1
C5	0.47µF	B2	CV2	30pF	B1
C6	0.1 uF	B2	CV3	80pF	B1
C7	220pF	B1	CV4	80pF	B1
C8	0.047µF	B2	CV5	30pF	A1
C9	0.47µF	B2	CV6	110pF	A1
C10	0.1 uF	B2			
C11	2.5µF	B2	Coils		
C12	0.01 µF	A1			
C13	0.01 µF	B2	L1	_	A1
C14	400µF	B2	L2	_	B1



_						A-1-1
	L3	_	A1	Miscellaneous		
	L4	_	B1			
	L5	_	A1	D1	BA114	B1
	L6		B2	S1-S7		A2
	L7		B2	TAD 100	_	B2
	L8	_	B2	LP1175	_	B2
	L9	5Ω	†			
				† Loudspeaker.		

TAD 100 voltage table

Tag	Volts	Tag	Volts	
1	_	8	1.5	7
2	7.2	9	7.5	
2	0.7	10	_	
4	1.9	11	2.0	
5	1.9	12	_	
6	5.2	13	1.3	
7	0	14	_	

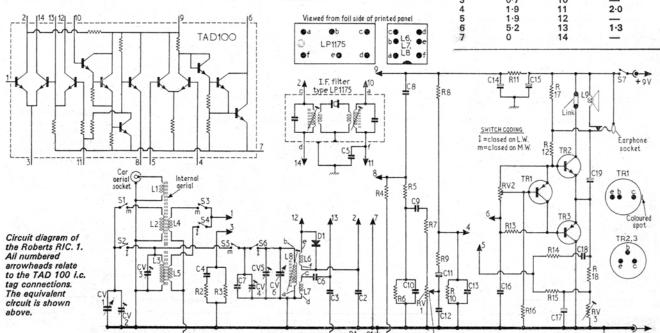

1884 Roberts RIC. 1

Continued from overleaf -

For these voltages to apply it is important that battery voltage of 9V measured across C15 is obtained, the quiescent current being 20mA. The TAD 100 integrated circuit can be checked completely from these d.c. parameters and it should not be suspect unless one or more of these voltages differs considerably from those in the table.

Circuit notes

Mullard TAD 100 silicon integrated circuit used in this receiver incorporates the mixer, oscillator, i.f. amplifier, a.g.c. and audio pre-amplifier stages. Reference to the equivalent circuit diagram shows that where coupled circuits occur within the i.c. they are d.c. couplings. It is because of the absence of a.c. couplings that the d.c. operating voltages are able to be used to determine whether the i.c. is functional or not.

If at any time it should become necessary to replace the i.c. the following precautions should be observed when handling the new i.c. capsule.

The device may be soldered directly into circuits with soldering irons. At bit temperatures below 245deg C the maximum soldering time should be less than ten seconds. Melting point of cored solder (60/40) is 190deg C, and as the temperature of the bit must be about 35-40deg C above this it means that a low power iron, say about 10W, should be used. If the bit temperature is between 245deg C and 400deg C, and this applies to most irons used, then the soldering time should be less than five seconds. Application of the soldering iron should always be below the seating plane (see illustration), and at no time should the device body temperature be allowed to exceed the maximum storage temperature which is 85deg C.

It is also necessary to take care not to bend the lead-out tags above the seating plane.

I.f filter module Mullard type LP1175 is a bandpass unit containing a ceramic resonator. The nominal frequency of the resonator is 470kc/s. This module establishes the bandwidth

of the i.f. amplifier and its centre frequency. It is important that the transformer cores are not disturbed unless suitable display equipment is available to ensure a symmetrical response curve.

Circuit alignment


Equipment required. — An r.f. signal generator amplitude modulated 30 per cent at 400c/s; an r.f. coupling coil and an audio output meter, impedance 5Ω or, alternatively, an a.c. voltmeter.

Connect the output meter in place of loudspeaker or the voltmeter in parallel with the loudspeaker. Check that with tuning gang at maximum capacitance, the pointer coincides with the low frequency end of the tuning scale. Rotate volume control to maximum, feed all signals in via the r.f. coupling coil, which should be loosely coupled to the ferrite rod aerial assembly, and maintain input signal at a level, such, that the a.g.c. remains inoperative. Alignment calibration marks are indicated on the scale at 1,224m and 1,936m.

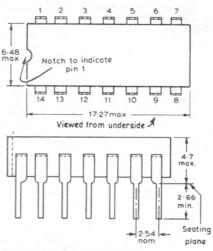- 1. Switch receiver to m.w., set tuning to 1,224m and feed in a 1,360kc/s a.m. signal. Adjust CV5 and CV2 for maximum output.
- 2. Set tuning to 1,936m and feed in a 580kc/s a.m. signal. Adjust **L8** and **L2** for maximum output.
- 3. Repeat operations 1 and 2 for optimum results finishing with 1.
- 4. Switch receiver to l.w., tune to 1,224m and feed in a 245kc/s a.m. signal. Adjust CV4 and CV3 for maximum output.
- Tune receiver to 1,936m and feed in a 155kc/s a.m. signal. Adjust L3 for maximum output.
- 6. Repeat operations 4 and 5 for optimum results finishing with 4.

General notes

Dismantling. – Disconnect and remove battery then loosen the three 4BA nuts securing the battery bracket and remove bracket. Unscrew and remove the two 4BA nuts securing the loudspeaker and carefully remove loudspeaker to the extent of its leads. Unscrew and remove two woodscrews at either side of chassis and withdraw the two wooden members. The chassis may now be gently slid out of the case.



Top and side views of the TAD 100 integrated circuit.

A.f. amplifier adjustments. – The following adjustments are to be carried out with a battery terminal p.d. of 9V measured across C15.

Connect a voltmeter between junction C19/R18 and chassis and, with volume control at minimum, adjust RV3 to produce 5·2V. Connect a milliammeter in the red flex link on the foil side of printed panel and adjust RV2 for an output stage quiescent current of 3·5mA at 20deg C, Allow one minute to elapse and recheck this figure. With an oscilloscope observe a sine-wave output and adjust RV3 for symmetry at onset of clipping.

Manufacturer's service department

Roberts Radio Company Limited, Molesey Avenue, West Molesey Surrey.

(Telephone: MOLesey 7474.)

